
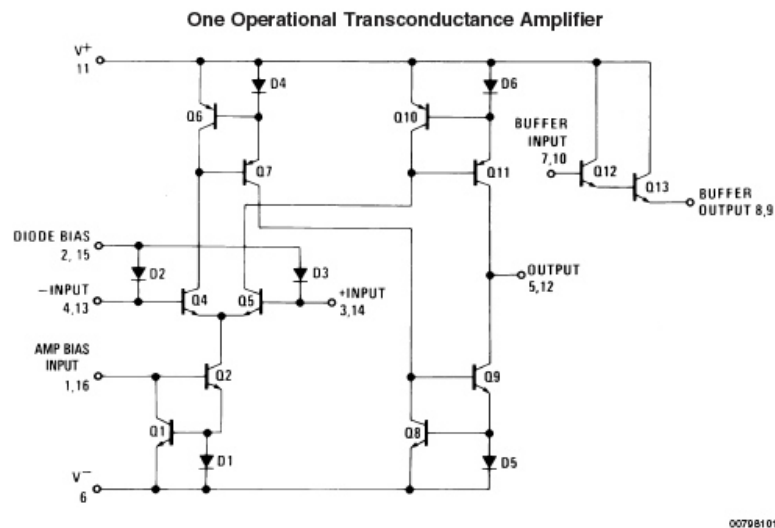


SUPPLEMENTAL LM13700 APPLICATION EXAMPLES

Schematic Diagram

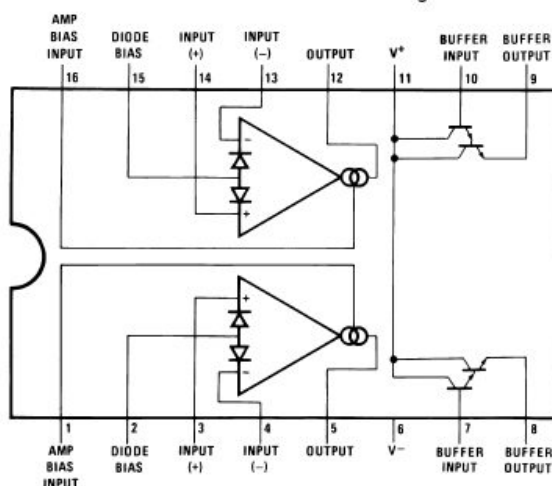

At the time when the LM13600/LM13700 datasheet was done, management was beginning to feel that the number of applications was getting out of hand. The LM13600/LM13700 data sheet was attempting to follow the LM3900 data sheet in that it now allowed customers to do things which up until then were not convenient. This application supplement attempts to add a few more examples as to how this Operational Transconductive Amplifier can be used.



This IC was some what done at the request of an Analog Organ manufacturer. Actually it was done as training lay out for a new mask designer. Some how it managed to get turned into an actual IC, which was very unusual. Marketing was not keen on supporting the creation of a new IC for a yet to be created market at that time.


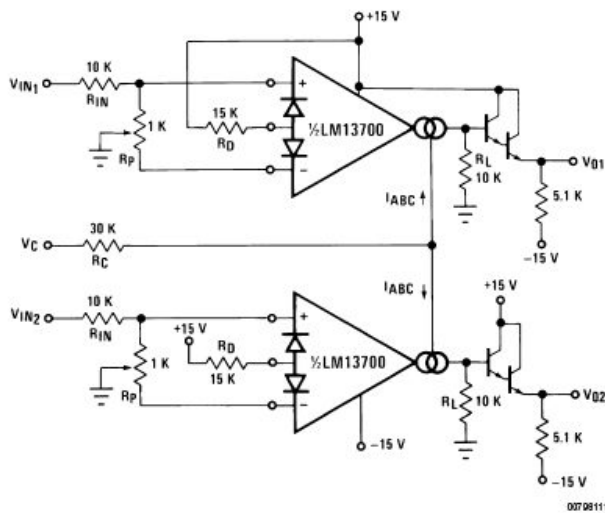



FIGURE 4. Stereo Volume Control

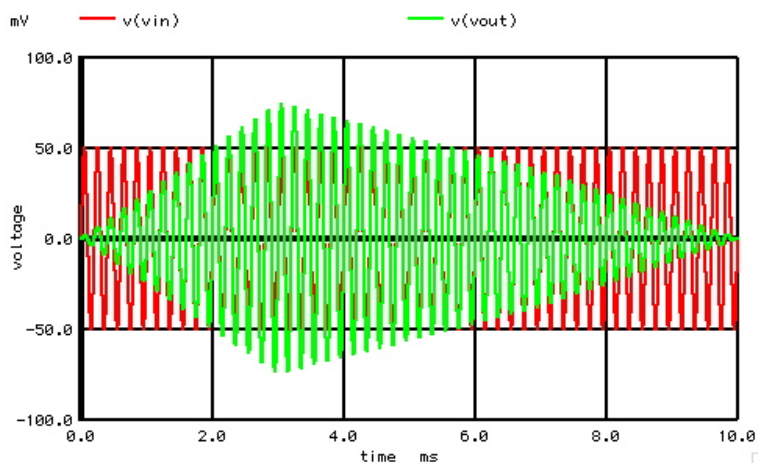Of course the first application was as a Voltage Controlled Amplifier. The Organ people needed to be able to adjust the attack and decay of a tone, and in spice today that can be simulated mathematically.



The whole Operational Transconductance Amplifier can be defined in one line..
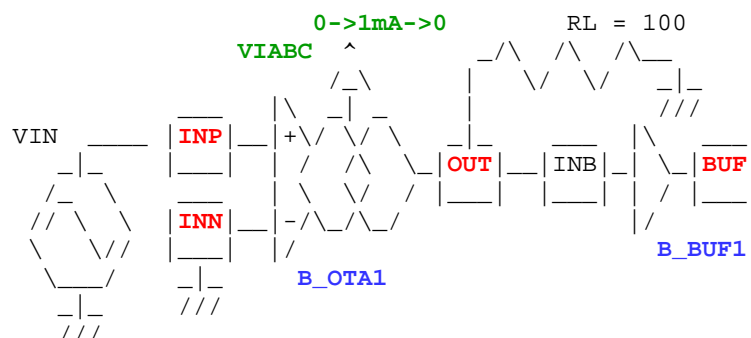
`B_OT1 OUT 0 I = -1*v(VIABC)*tanh((v(INP)-v(INN))/0.052)`



Where a PWL source (**VIABC**) is set to track IABC over time...


V_labc **VIABC** 0 **PWL** (0m 0m 3m 1m 10m 0m)

There is an extra feature in that the definition of the buffer need not include offset.

B_BUF1 **BUF** 0 **V** = **v(OUT)** or ...
B_BUF1 **BUF** 0 **V** = **v(OUT)** -1.2V

This can make the [spice netlist of attack and decay simulations](#) extremely simple.


Typical Application

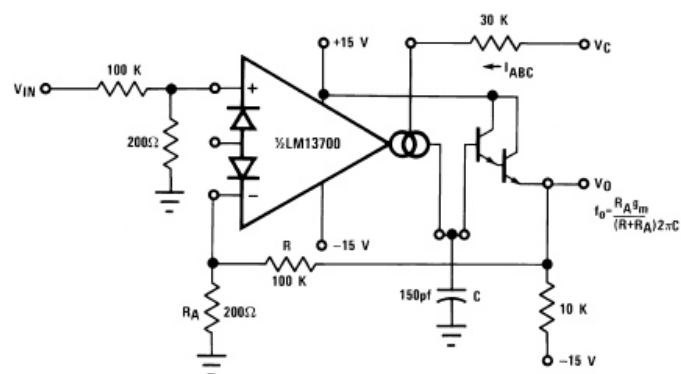

Voltage Controlled Low-Pass Filter

00798118

The data sheet lists a [voltage control lowpass filter](#) as a typical application because of a home Hi Fi project. The idea was to adjust the bandwidth of the audio channel to always match the bandwidth of the music. A noticeable reduction in noise for cassette tapes was the result. The Home project work so well that Delco decided to use it instead of Dolby. More information on this can be found at [Wikipedia](#).

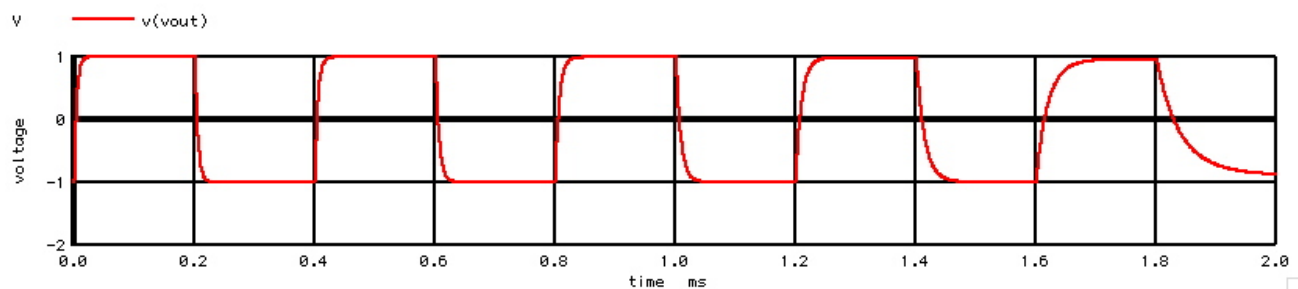

Another application for this circuit could be as a Voltage Follower which has a [Voltage Controllable Time Constant](#). Perhaps one might want an envelope with a slow or fast attack and a fast or slow decay.

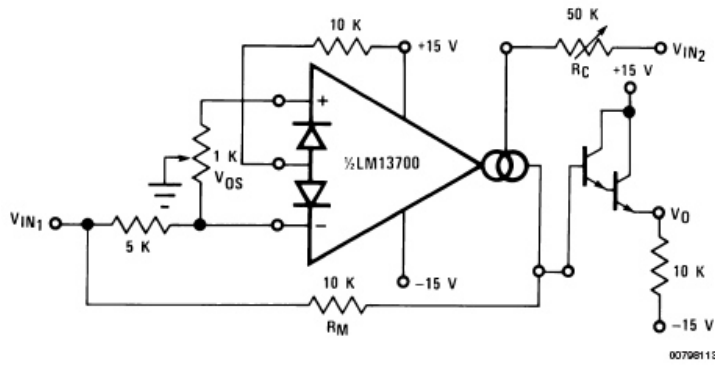


FIGURE 6. Four-Quadrant Multiplier

In some cases the [Four-Quadrant spice simulation](#) might make the data sheet schematic a little easier to understand.

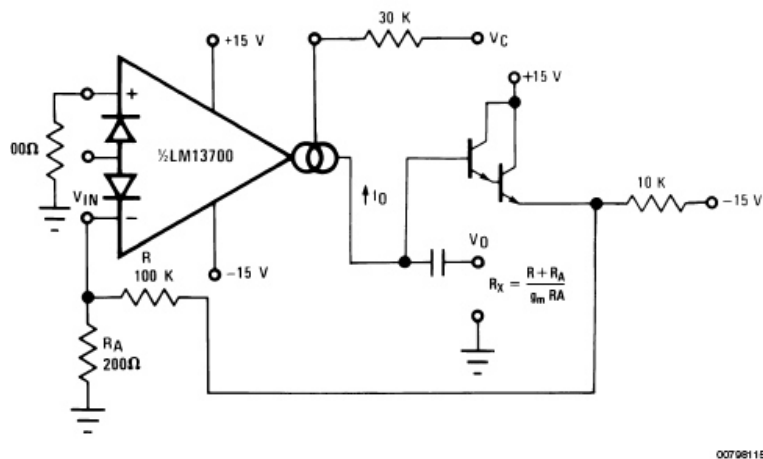


FIGURE 8. Voltage Controlled Resistor, Single-Ended

For the [Voltage Controlled Resistor](#) application, being able to simulate using perfect buffers instead of darlingtontons has its advantages. This is especially true when it comes to building [Voltage Controlled Capacitors](#) and [Voltage Controlled Inductors](#).



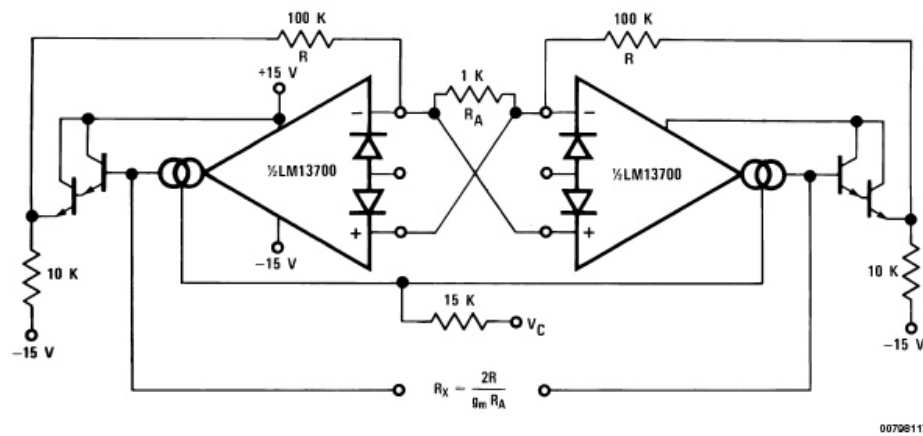


FIGURE 10. Floating Voltage Controlled Resistor

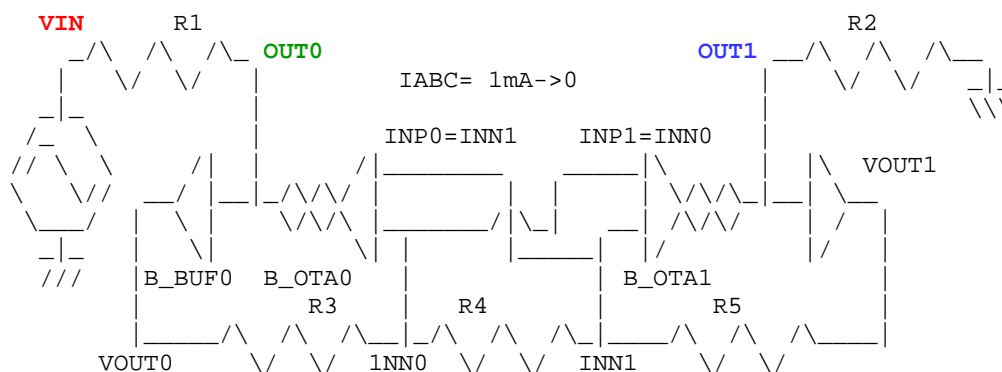The [Floating Voltage Controlled Resistor](#) functions just fine with the darlington 1.2V offsets. The simulation of this circuit shows why. To see the floating resistor in action, the example needs to be put into a resistor network.



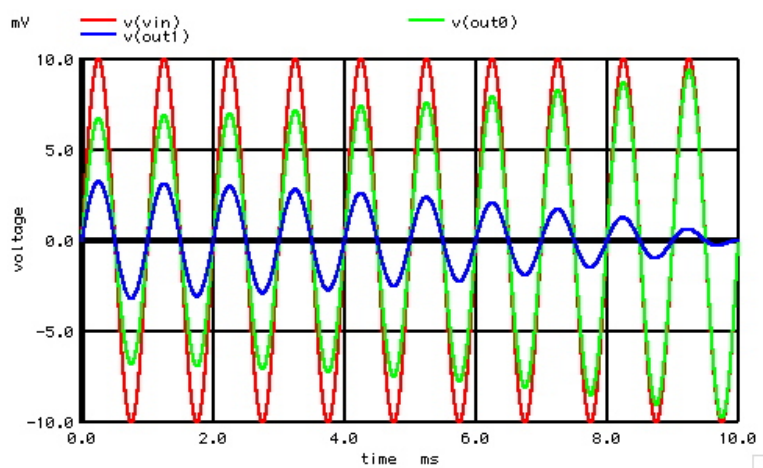With IABC going from 1mA to zero, the floating resistor appears to be going from 10K Ohms to Open. The wave forms below shows that.



But any type of Voltage Controlled Impedance can be made using OTAs. A [Voltage Controlled Negative Resistor](#) can cancel out the current loading of a Load Resistor. And a [Voltage Controlled Negative Capacitor](#) can cancel out stray capacitance to greatly improve speed.

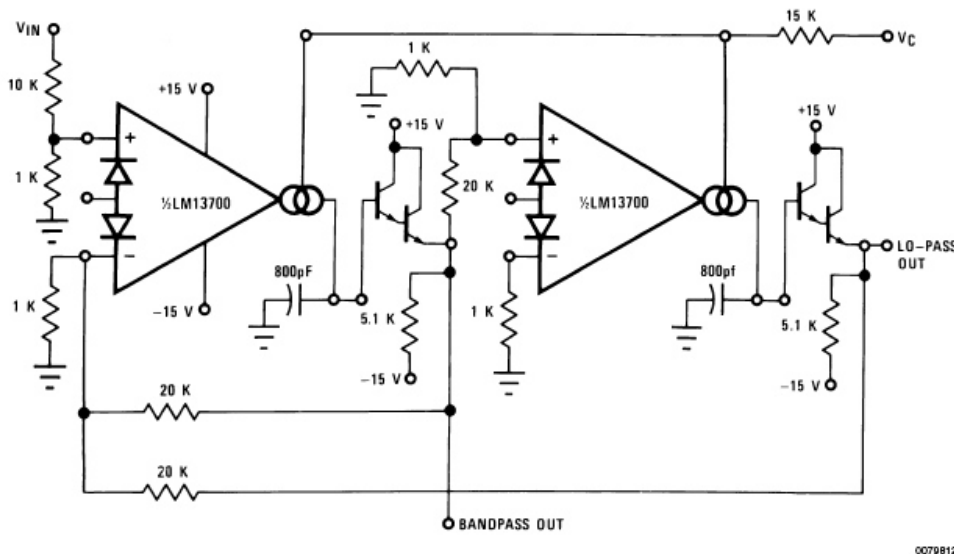


FIGURE 14. Voltage Controlled State Variable Filter

The [State Variable Filters](#) are by far the most beautiful of all the filters. Different filters can be made simply by changing voltage feedback. For instance a [Bessel filter](#) has a set of feedbacks such that a low pass filter signal is not shaped distorted. If maximally flat gain is required, then the feedback can be adjusted to form a [Butterworth filter](#).

Regardless of type of filter, the frequency response is independently controllable

over up to maybe 5 orders of magnitude for the LM13600 (not LM13700) and may get as high a 10-12 orders of magnitude in frequency if it were built in BiCMOS today.

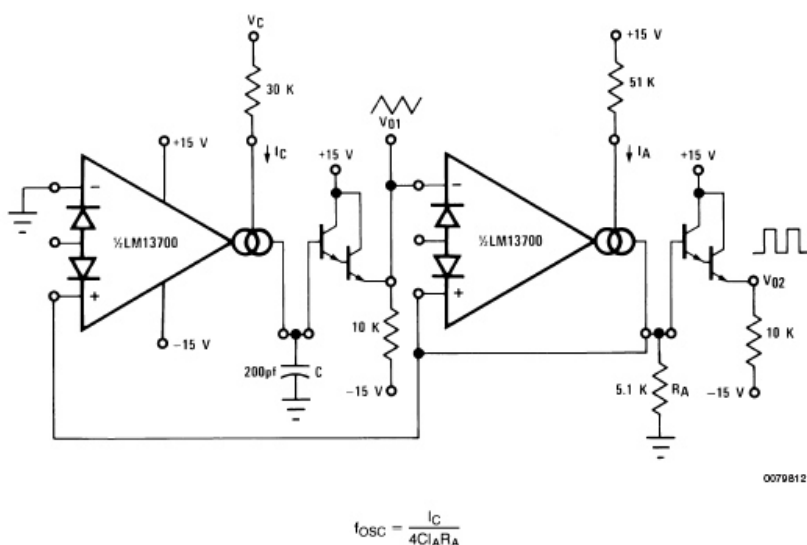


FIGURE 15. Triangular/Square-Wave VCO

The [circuit above can come in very handy in a lab](#) which tends to have

should also be a sine wave output.



$$V_{PK} = \frac{(V^+ \pm 0.8V) R_2}{R_1 + R_2}$$

$$t_H \approx \frac{2V_{PK}C}{I_F}$$

$$t_L \approx \frac{2V_{PK}C}{I_C}$$

$$f_0 \approx \frac{I_C}{2V_{PK}C} \text{ for } I_C < I_F$$

FIGURE 16. Ramp/Pulse VCO


some timing applications




FIGURE 22. Schmitt Trigger

There are a whole class of nonlinear relationships that one encounters applying electronics to the real world. The Schmitt Trigger application was an attempt to investigate this area. The following are some of these nonlinear relationships


listed
under their common system names.

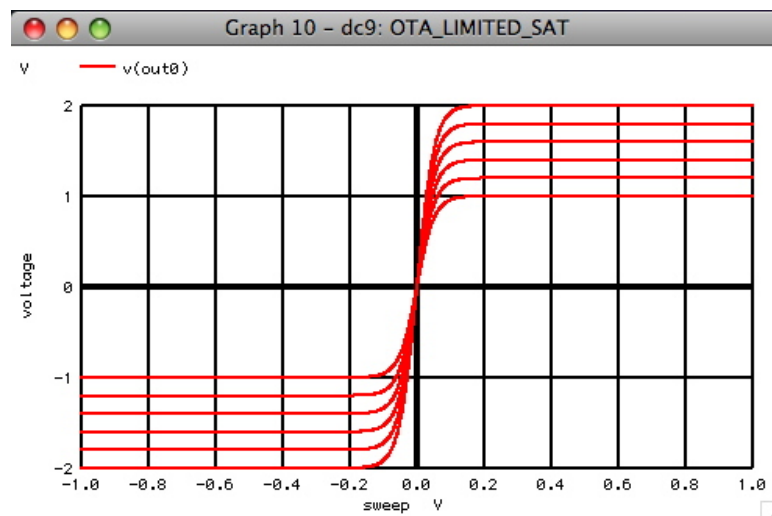

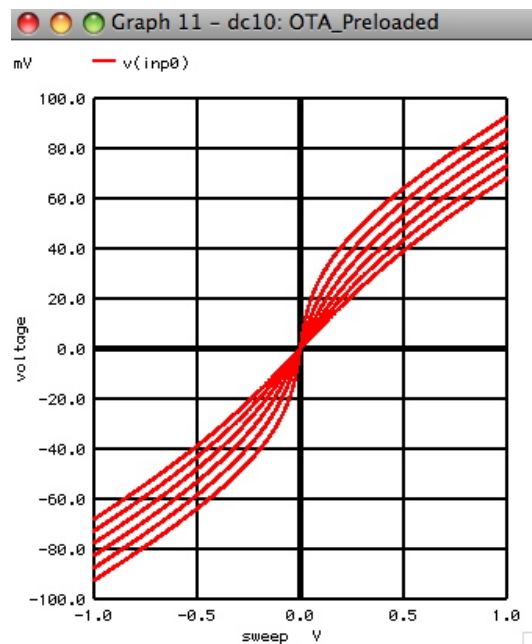
The [limited Saturation](#) is of course the natural nonlinearity of OTAs. This nonlinearity together with other types of nonlinearity may allow good modeling of a saturating magnetic core.



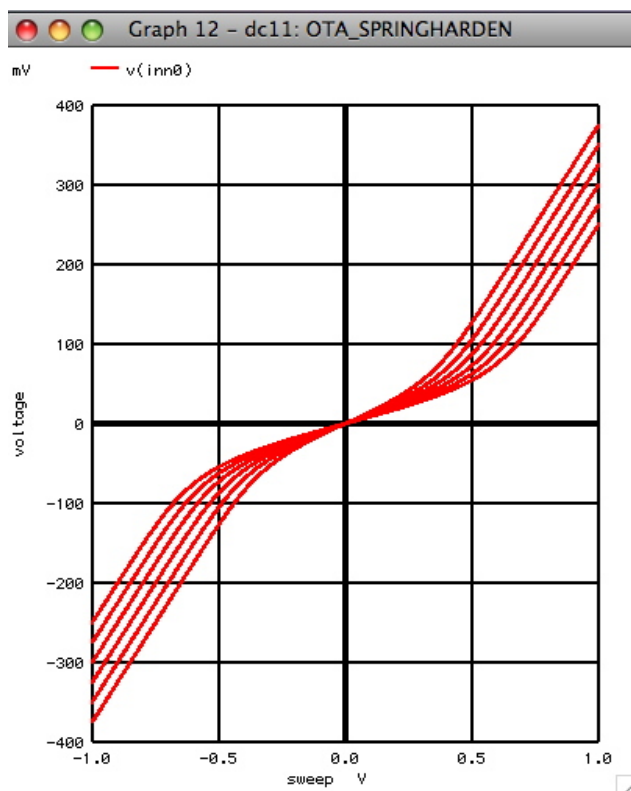
[Preloaded](#) means something is under stress without an external load.



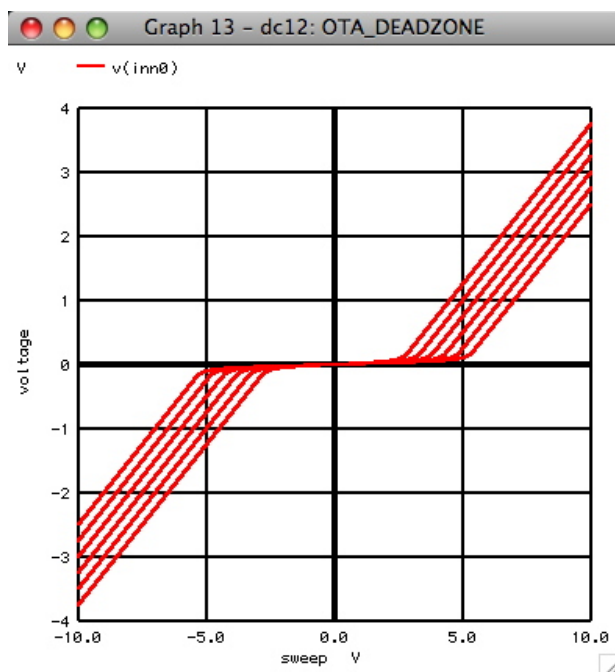This one is called [Spring Hardening](#).



This is called [Dead Zone](#).

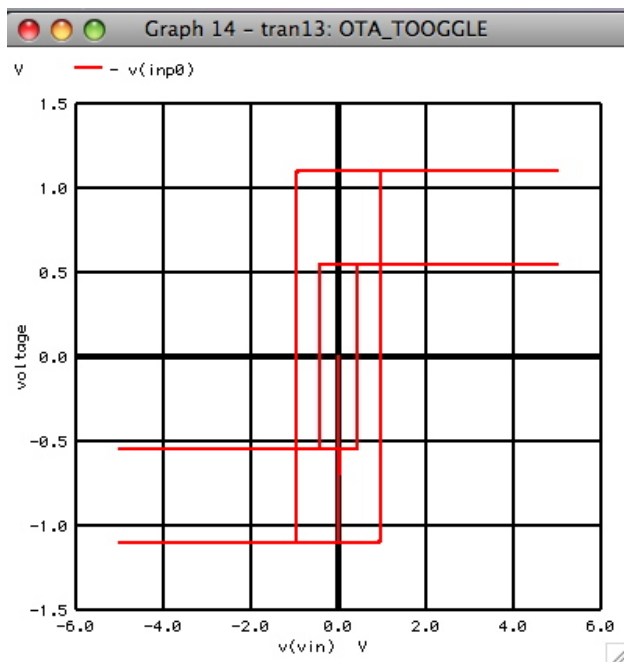

The [Toggle](#) which is also the schmitt trigger application has memory of its past input signal built in. Combining this feature with some of the other nonlinearities may allow close modeling of magnetic components.